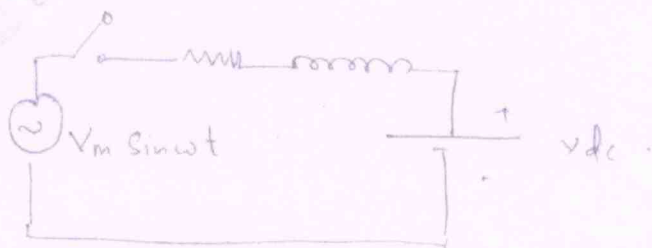


Q1



(a) STEADY STATE CURRENT :

By Superposition, considering only AC source




At steady state,

$$i_{ac} = \frac{V_m \sin(\omega t - \phi)}{\sqrt{\omega^2 L^2 + R^2}}$$

where $\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$ [1 mark]

Considering only DC source,

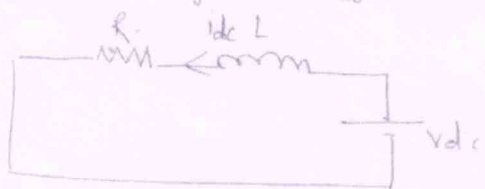

At steady state, inductor acts as short

circuit for DC

$$i_{dc} = + \frac{V_{dc}}{R}$$

[1 mark]

Net current at steady state

$$i = i_{ac} - i_{dc} = \frac{V_m \sin(\omega t - \phi)}{\sqrt{\omega^2 L^2 + R^2}} - \frac{V_{dc}}{R}$$

[1 mark]

(b) for $t > 0$,

$$i(t) = \frac{V_m \sin(\omega t - \phi)}{\sqrt{\omega^2 L^2 + R^2}} - \frac{V_{dc}}{R} + k e^{-t/\tau}$$

at $t = 0$, $i = 0$

[1 mark]

$$0 = \frac{V_m \sin(-\phi)}{\sqrt{\omega^2 L^2 + R^2}} - \frac{V_{dc}}{R} + k$$

$$i = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin \phi + \frac{V_{dc}}{R} \quad \left[1 \text{ mark} \right]$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t - \phi) - \frac{V_{dc}}{R} + \left[\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_{dc}}{R} \right] e^{-Rt/L}$$

Q2.


$$\begin{aligned}\bar{I}_{in} &= \frac{\bar{V}_o}{4} + \frac{\bar{V}}{4j} - \frac{\bar{V}_o}{4j} \\ &= \frac{\bar{V}_o}{4}\end{aligned}$$

1 mark

$$\begin{aligned}4\text{mH} &= 4 \times 10^{-3} \times 1000 \Omega \\ &= 4 \Omega \\ 0.2\text{mF} &= \frac{1}{1000 \times 0.2 \times 10^{-3}} \\ &= 4 \Omega\end{aligned}$$

$$\bar{V}_o = 4 \bar{I}_{in}$$

2 mark

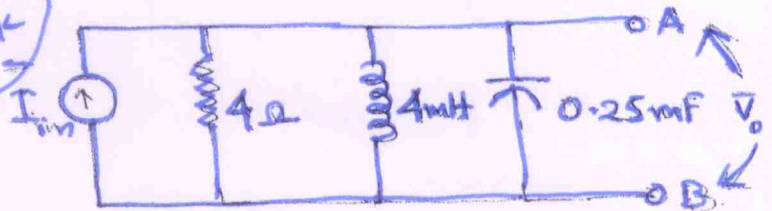

$$= 4 \cdot 2 \angle 45^\circ = 8 \angle 45^\circ$$

$$V_o = 8\sqrt{2} \cos(1000t + 45^\circ)$$

$$= 11.313 \cos(1000t + 45^\circ)$$

$$Z_{th} = 4 + j0$$

$$= 4 \angle 0^\circ$$

2 mark.

Q3.

Taking the current as the reference phasor, the ~~se~~ phasor diagram of the circuit is ~~is~~ shown in the figure assuming V_L to be the voltage drop across the inductor.

$$\therefore (230)^2 = (200 - V_L)^2 + 20^2$$

$$\therefore V_L^2 - 400V_L - 12500 = 0$$

$$\therefore V_L = 429.12, -29.12$$


Negative of V_L means it is lagging I by an angle 90°

not possible for an inductor, hence this negative value is discarded.

$$\therefore V_L = 429.12 \text{ V}$$

$$\therefore I = \frac{429.12}{100} = 4.29 \text{ A}$$

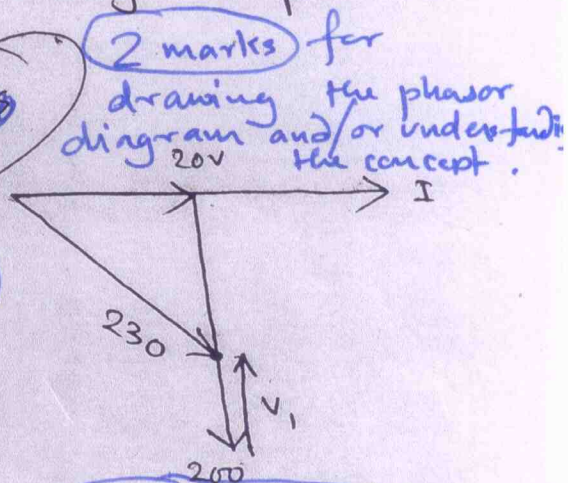If no reasoning is provided why the +ve value is considered deduct 1 mark



2 marks for taking the decision of +ve/-ve which is

2 marks


Q4. Time period of p is 5ms, therefore $f = 200 \text{ Hz}$

Frequency of the source is therefore $\frac{200}{2} \text{ Hz} = 100 \text{ Hz}$
1 mark.

Let the equation of the instantaneous power is:

$$p = X \sin \omega t + y \text{ --- (1)}$$
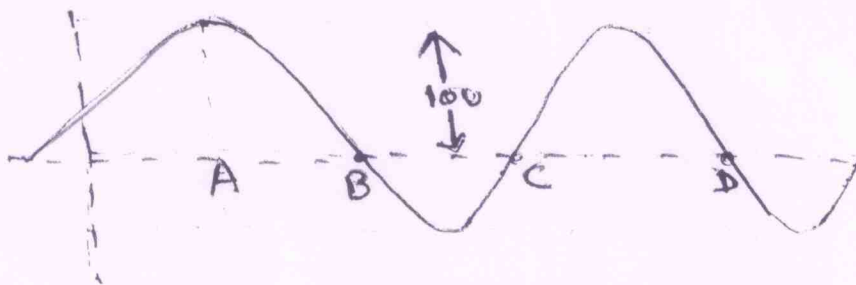
$$\omega = 2\pi f = 2 \times \pi \times 200 = 1256.637$$



$$AD = AB + BC + CD = 5 \text{ ms}$$

$$\text{or, } 2AB + BC = 5 \text{ ms}$$

$$\therefore 2AB = (5 - 1.666) \text{ ms or, } AB = 1.667 \text{ ms}$$

Considering (1) P_{max} will occur at $\omega t = \pi/2$ or $t = 1.25 \text{ ms}$

$$\therefore 100 = X + y \text{ --- (2)}$$

$$p = 0 \text{ will be at } t = (1.25 + 1.667) \text{ ms} = 2.917 \text{ ms}$$

$$\therefore 0 = X \sin (1256.637 \times 2.917 \times 10^{-3}) + y$$

$$\text{or, } 0 = -0.5X + y \text{ --- (3)}$$

$$\text{Solving (2) and (3), } X = 66.67, \quad y = 33.33$$

The average value of the waveform = power = 33.33 watt.


$$\therefore \text{Now } \phi = 1.667 \times \frac{360}{10} = 59.97 \approx 60^\circ$$

$$VI \cos \phi = 33.33 \Rightarrow VI = \frac{33.33}{0.5}$$

$$\therefore \text{Reactive power} = VI \sin \phi = 66.66 \sin 60^\circ = 57.27 \text{ VAR}$$

4 marks

(Q5)

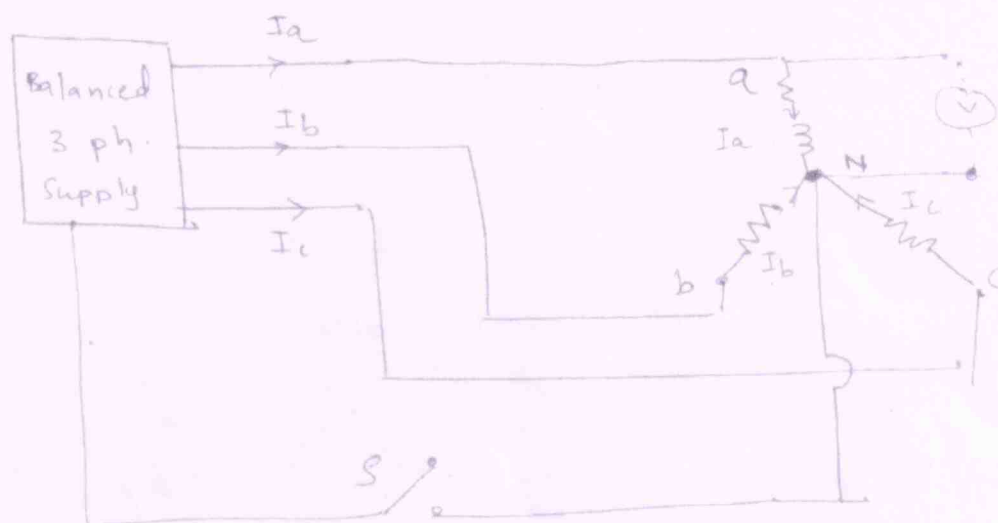

- (1) S is closed \Rightarrow Load neutral is at same potential as supply neutral.

Balanced voltages appear across load

$$V_{an} = \frac{400}{\sqrt{3}} = 230.9 \text{ V}$$

$$\boxed{V_{an} = 230.9 \angle 0^\circ, \quad V_{bn} = 230.9 \angle -120^\circ}$$
$$\& \quad V_{cn} = 230.9 \angle 120^\circ$$

$$I_N = I_a + I_b + I_c$$

$$= \frac{V_{an}}{10 + j10} + \frac{V_{bn}}{10} + \frac{V_{cn}}{10}$$


$$\boxed{I_N = 16.33 \angle -135^\circ} \leftarrow \boxed{\text{mark}}$$

5) ②

's' is open

⇒ Load and supply neutrals are not connected

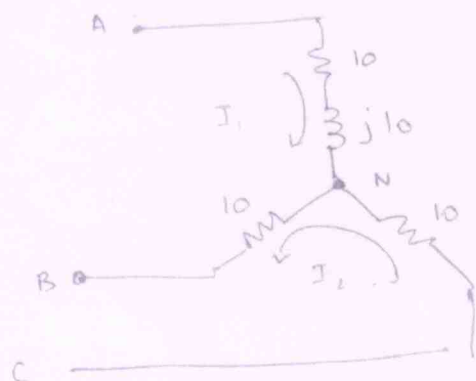⇒ Load phase-neutral voltages are NOT balanced



$$V_{AB} = \bar{I}_1 (10 + j10) + (\bar{I}_1 + \bar{I}_2) 10 = 400 \angle 0$$

$$V_{CB} = 10 \bar{I}_2 + (\bar{I}_1 + \bar{I}_2) 10 = -400 \angle -120$$

Solving,

$$2\bar{I}_1 (10 + j10) + 20 \bar{I}_1 + 20 \bar{I}_2 - 20 \bar{I}_2 - 10 \bar{I}_1 =$$

$$800 \angle 0 + 400 \angle -120$$

$$30 \bar{I}_1 + j \bar{I}_1 (20) = 800 \angle 0 + 400 \angle -120$$

$$\bar{I}_1 = \frac{800 \angle 0 + 400 \angle -120}{30 + j20}$$

$$= 19.21 \angle -63.69^\circ \text{ A}$$

2 marks
(steps)

and $V_1 = \bar{I}_1 (10 + j10)$


$$= \boxed{271.63 \text{ V}} \leftarrow \boxed{1 \text{ mark}}$$

(Q6)


Three reading of wattmeter

(ia) $(V_{BC}) = \cos(\theta)$

angle betw V_{Aa} & V_{BC} .

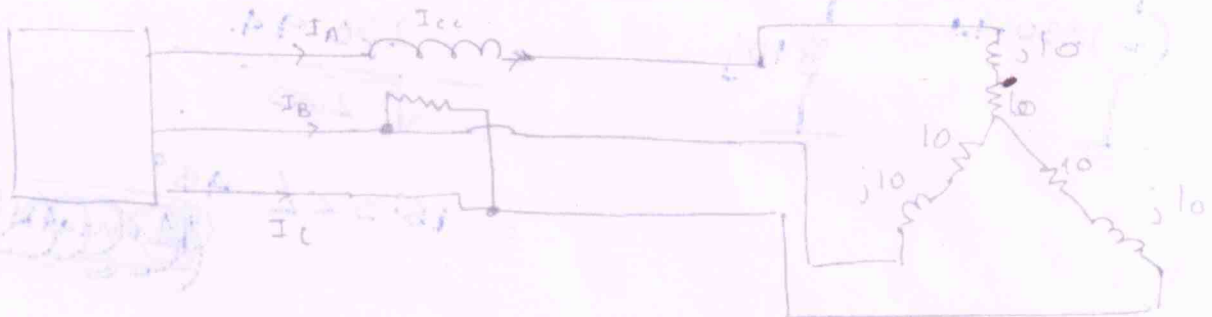

(2 marks)

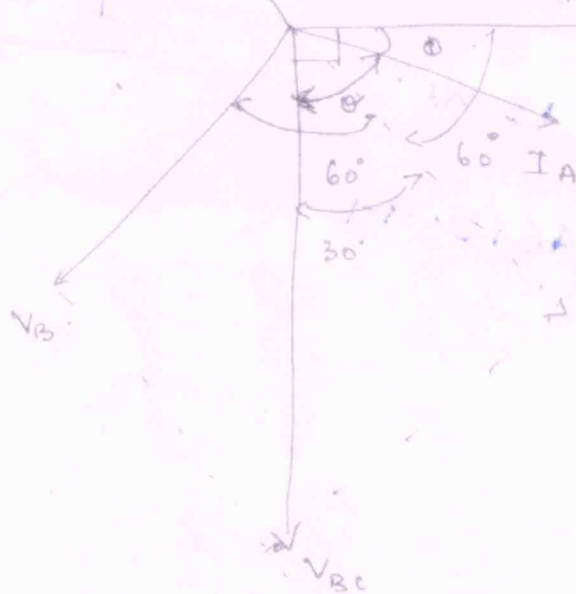

$$\theta = 90 - \phi$$

$$W = I_A V_{BC} \cos(90 - \phi)$$

$$= I_A V_{BC} \sin \phi$$

$$= \sqrt{3} V_{ph} I_{ph} \sin \phi$$

$$\tan \phi = \frac{10}{10} = 1$$

2 marks

$$\sin \phi = 1/\sqrt{2}$$

$$|I| = \frac{230.94}{\sqrt{10^2 + 10^2}} = 16.32$$


1 mark

$$W = \sqrt{3} \times 230.94 \times 16.32 \times \sin(45)$$

$$= 4615.99$$

1 mark

Per phase equivalent ckt:

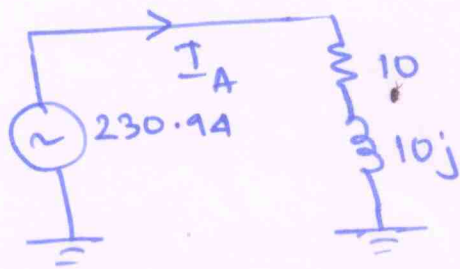

$$\begin{aligned} I_A &= \frac{230.94}{\sqrt{10^2 + 10^2} \angle 45^\circ} \\ &= \frac{230.94}{\sqrt{200}} \\ &= 16.32 \angle -45^\circ \end{aligned}$$

~~1 mark~~

$$\begin{aligned} \therefore P_{\text{gen}} &= \sqrt{3} \times 400 \times 16.32 \times \cos 45^\circ \\ &= 7995.13 \text{ W.} \end{aligned}$$

1 mark.

$$\begin{aligned} \text{Reactive} &= \sqrt{3} \times 400 \times 16.32 \times \sin 45^\circ \\ &= 7995.13 \text{ W} \\ &= \sqrt{3} \times 4615.99 \end{aligned}$$

1 mark.


1 mark.

1 mark.

1 mark.

1 mark.

Q7.

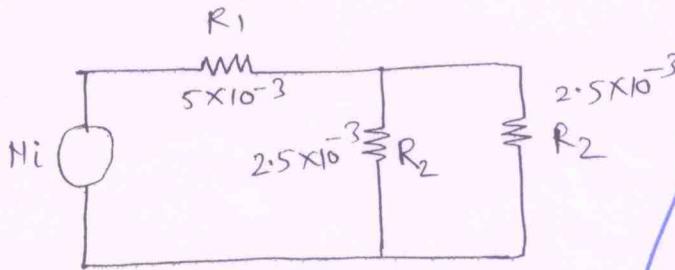

$$R_1 = \frac{24 \times 10^{-2}}{4 \times 12 \times 10^{-4}}$$

$$R_2 = \frac{72 \times 10^{-2}}{4 \times 6 \times 10^{-4}}$$

$$\phi = \frac{\text{MMF}}{R}$$

1 mark.

$$\text{mmf required for } R_1 = \frac{24 \times 10^{-2}}{4 \times 12 \times 10^{-4}} \times 5 \times 10^{-3}$$

1 mark

$$\text{mmf required for } R_2 = \frac{72 \times 10^{-2}}{4 \times 6 \times 10^{-4}} \times 2.5 \times 10^{-3}$$

1 mark

$$\frac{24 \times 5 \times 10^{-5}}{4 \times 12 \times 10^{-4}} + \frac{72 \times 2.5 \times 10^{-5}}{4 \times 6 \times 10^{-4}} = 750 \times 0.5$$

$$\frac{1}{4} + \frac{72 \times 2.5}{4 \times 60} = 375$$

$$\frac{1}{4} [1 + 3] = 375$$

$$\frac{4}{4} = 375$$

$$4 = \frac{4}{375} \approx 0.01066$$

$$\mu_0 \mu_r = \frac{4}{375}$$

$$\mu_r = \frac{4}{375 \times 4\pi \times 10^{-7}} = 8488.26$$

3 marks

For calculation mistake deduct 1 mark.