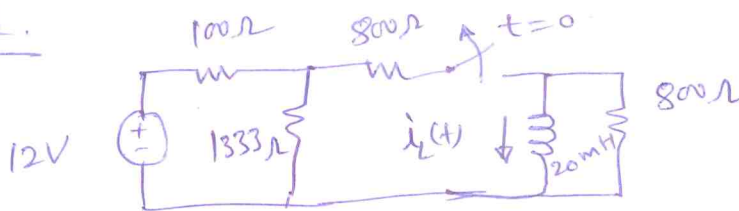



Assignment-2

①

Ques 1.



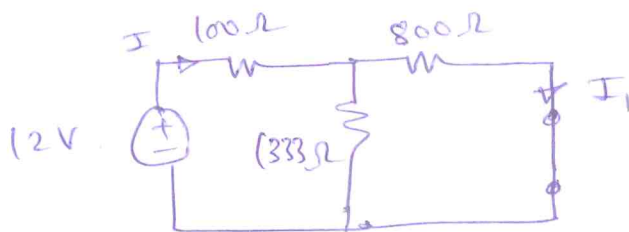∵ 12-V source has been applied for a long time before the switch open at $t=0$. So the inductor will behave as short circuited prior to $t=0$.
And above circuit will look as -



Resistance seen by the 12-V source

$$= 100 + \frac{1333 \times 800}{1333 + 800} = 600 \Omega$$

$$I = \frac{12}{600} = 0.02 \text{ A}$$


Current through inductor

$$I_L = 0.02 \times \frac{1333}{1333 + 800} = 0.01249 = 12.5 \text{ mA}$$

$$\text{So } \boxed{I_L(0^+) = 12.5 \text{ mA}}$$

when switch is opened at $t=0$. the ckt to find inductor will be as -

(2)

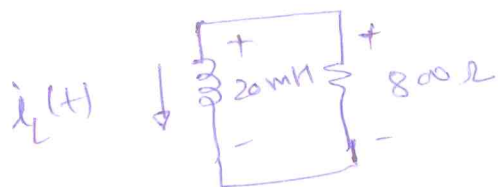

writing KVL

$$v_L(t) + R \times i_L(t) = 0$$

$$v_L(t) = -R i_L(t)$$

$$L \frac{di_L(t)}{dt} = -R i_L(t)$$

$$\frac{di_L(t)}{i_L(t)} = -\frac{R}{L} dt$$

Integrating both the sides.

$$\log i_L(t) = -\frac{R}{L}t + K$$

$$i_L(t) = e^{(-R/L)t + K}$$

$$i_L(t) = e^{-R/Lt} e^K$$

$$i_L(t) = e^{-R/Lt} C$$

 $C = e^K = \text{constant.}$

which we find by initial condition.

$$12.5 \text{ mA} = e^{-R/L \times 0} C$$

$$C = 12.5 \text{ mA}$$


 $R = 800 \Omega$ & $L = 20 \text{ mH}$

$$\text{So } i_L(t) = 12.5 e^{-800/20 \times 10^{-3} t}$$

$$i_L(t) = 12.5 e^{-40000t} \text{ mA for } t > 0$$


Sketch of $i_L(t)$ —

(in mA)

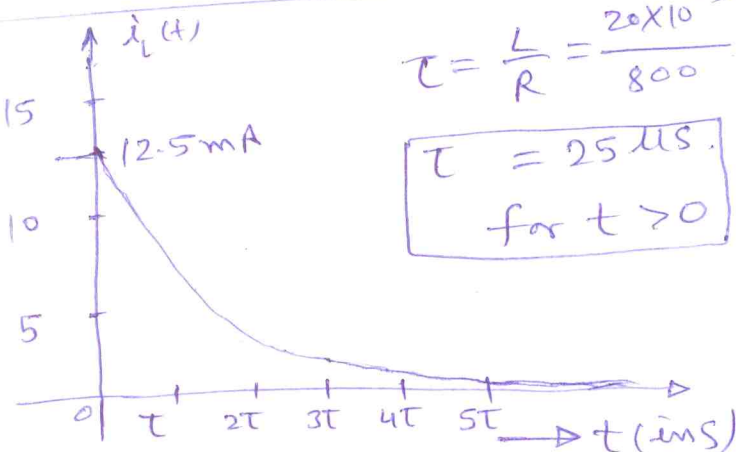


Que 2. a


3

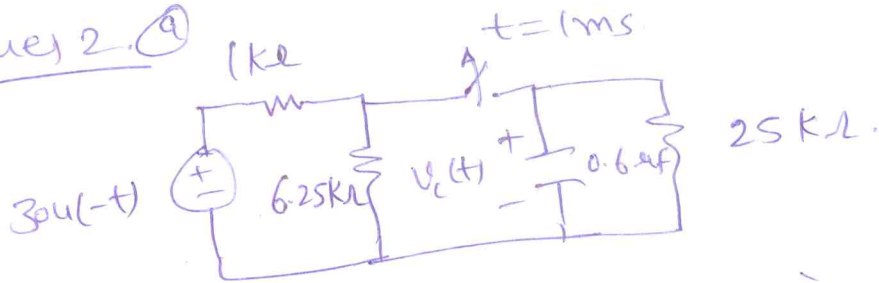


The waveform of $30u(-t)$ is as

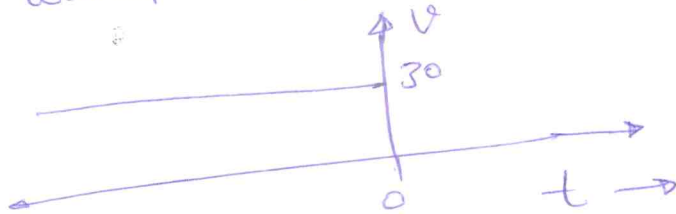

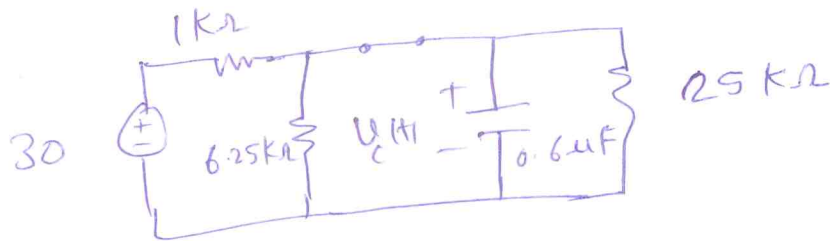So Above circuit prior to $t=0^+$ will be as.



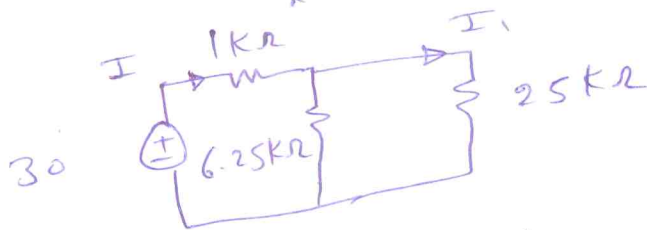The capacitor will act as open circuited so voltage across it will be the same which will be $25k\Omega$ resistance at $t=0^-$.



Resistance seen by 30V is

$$R = 1k\Omega + \frac{6.25 \times 25}{6.25 + 25} k\Omega$$

$$= 6k\Omega$$

$$I = \frac{30}{6k\Omega} = 5mA$$

$$I_1 = 5 \times \frac{6.25}{6.25 + 25} = 1mA$$


Voltage across $25\text{K}\Omega$ resistor

$$= 25\text{K}\Omega \times 1\text{mA} = 25\text{V}.$$


So it is the same across cap at $t=0^+$

$$V_c(t=0^+) = 25\text{V}$$

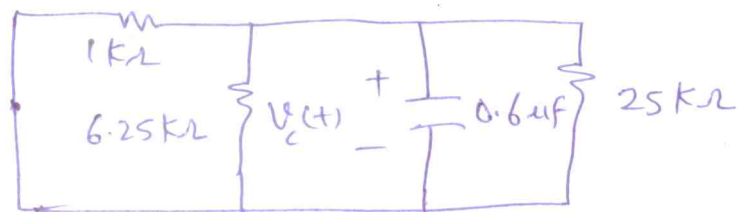At $t=0$ the voltage source vanishes & following circuit remains till $t=1\text{ms}$.



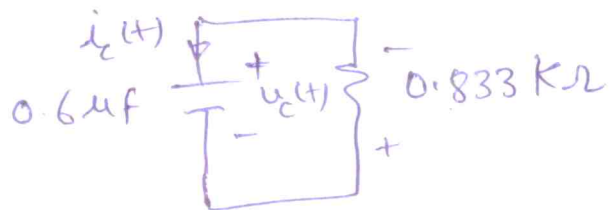\therefore All the resistance are in parallel to capacitor.
So following eq. circuit results



writing KVL

$$V_c(t) + R i_c(t) = 0$$

$$V_c(t) + RC \frac{dV_c(t)}{dt} = 0$$

$$\frac{dV_c(t)}{dt} = -\frac{1}{RC} V_c(t)$$

$$\frac{dV_c(t)}{V_c(t)} = -\frac{1}{RC} dt$$

Integrating on both the sides.

(5)

$$\log v_c(t) = -\frac{1}{RC}t + k$$

$$v_c(t) = e^{-t/RC} e^k$$

Again the constant is find out by initial Condition.

$$25 = e^{-0/RC} \times e^k$$

$$e^k = 25$$

So
$$v_c(t) = 25 e^{-t/(0.833 \times 0.6 \times 10^{-3})}$$


$v_c(t) = 25 e^{-2000t} \text{ V}$	$0 < t < 1 \text{ ms}$
------------------------------------	------------------------

(6)

$$\begin{aligned} v_c(1^+ \text{ ms}) &= v_c(1^- \text{ ms}) \\ &= 25 e^{-2000 \times 1 \times 10^{-3}} \end{aligned}$$

$v_c(1^+ \text{ ms}) = 3.383 \text{ V}$

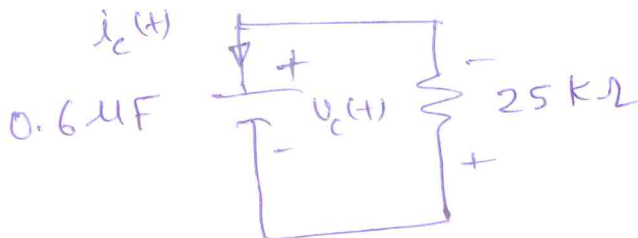Now for $1 \leq t \text{ ms}$ the circuit will be as-



$$v_c(t) + \cancel{25000} i_c(t) = 0$$

$$v_c(t) + \cancel{25000} RC \frac{dv_c(t)}{dt} = 0$$

$$\frac{dv_c(t)}{dt} = -\frac{1}{RC} v_c(t)$$

$$\int_{V_c(t)}^{V_c(t)} \frac{dV_c(t)}{V_c(t)} = \int_{t=1\text{ms}}^t -\frac{1}{RC} dt$$

$$V(1\text{ms}) = 3.383$$

$$\left[\log V_c(t) \right]_{3.383}^{V_c(t)} = -\frac{1}{RC} (t - 0.001)$$

$$\log [V_c(t) - 3.383] = -\frac{1}{RC} (t - 0.001)$$

$$V_c(t) = 3.383 e^{-(t-0.001)/RC}$$


$$\text{where } R = 25\text{ k}\Omega, C = 0.6\text{ }\mu\text{F}$$

$$\tau = RC = 25 \times 0.6 \times 10^{-3} = 0.015\text{ s}$$

$$V_c(t) = 3.383 e^{-\frac{(t-0.001)}{0.015}} \text{ V} \cdot 1 \leq t \text{ ms}$$


(c)

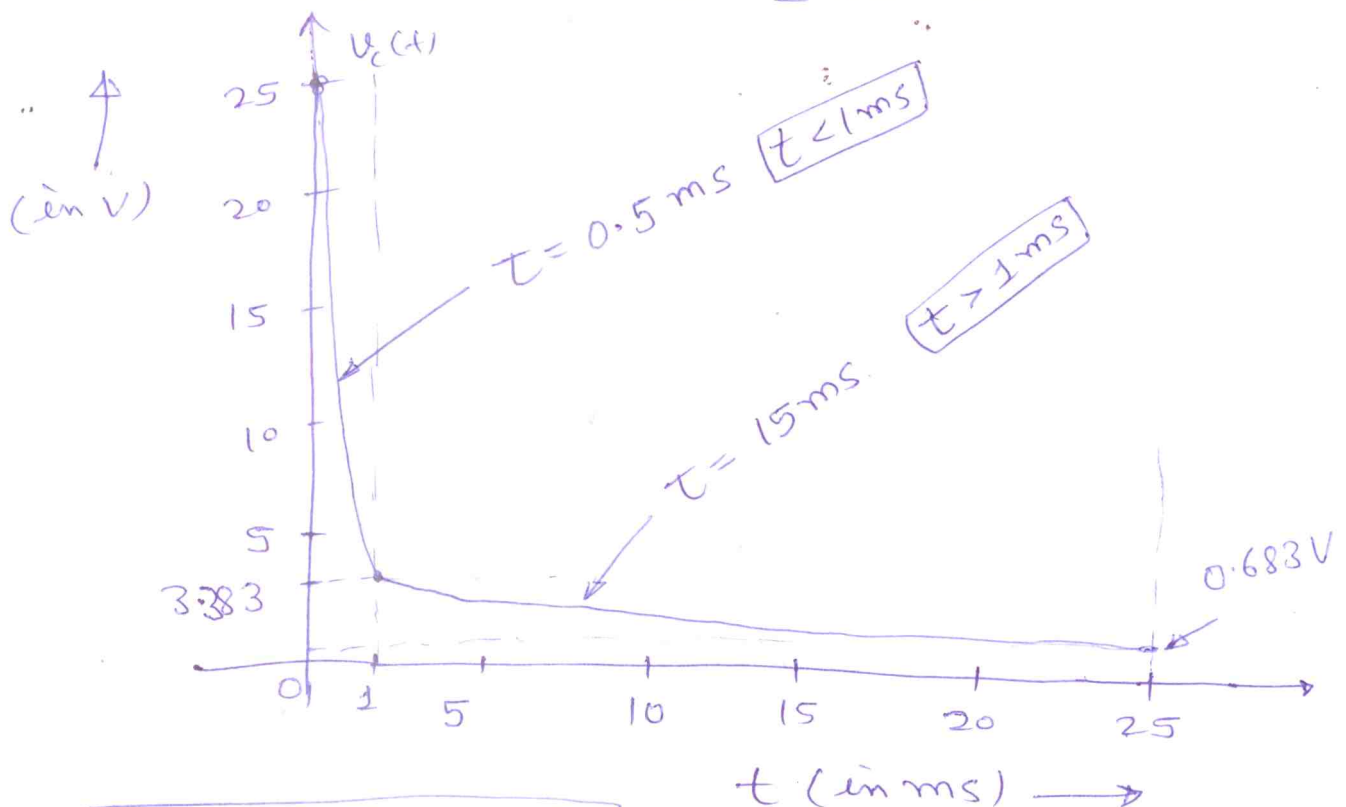Sketch $V_c(t)$ for $0 \leq t \leq 25\text{ ms}$



$$V_c(25\text{ms}) = 0.683\text{ V}$$

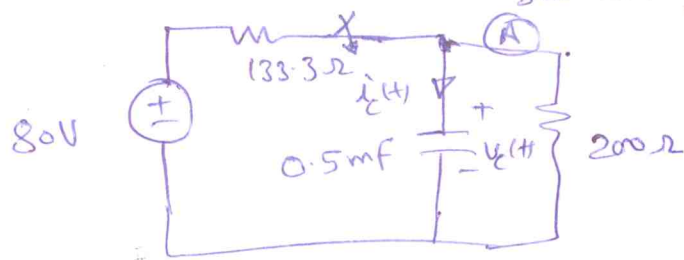Que 3 (a) when $t=0$ the switch is closed



for $0 \leq t \leq 0.06$ s writing KCL at node A

$$\frac{V_c(t) - 80}{133.3} + i_c(t) + \frac{V_c(t)}{200} = 0$$

$$\frac{V_c(t) - 80}{133.3} + C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{200} = 0$$

$$0.04 \frac{dV_c(t)}{dt} + V_c(t) = 48$$

$$V_c(t) = 48 (1 - e^{-t/0.04})$$

$$V_c(t) = 48 (1 - e^{-25t})$$


$$0 \leq t \leq 60 \text{ ms}$$

$$V_c(t) = V_c(0.06)$$

$$= 48 (1 - e^{-25 \times 0.06})$$

$$V_c(t) = 37.29 \text{ V}$$

Circuit for $t \geq 60 \text{ ms}$.

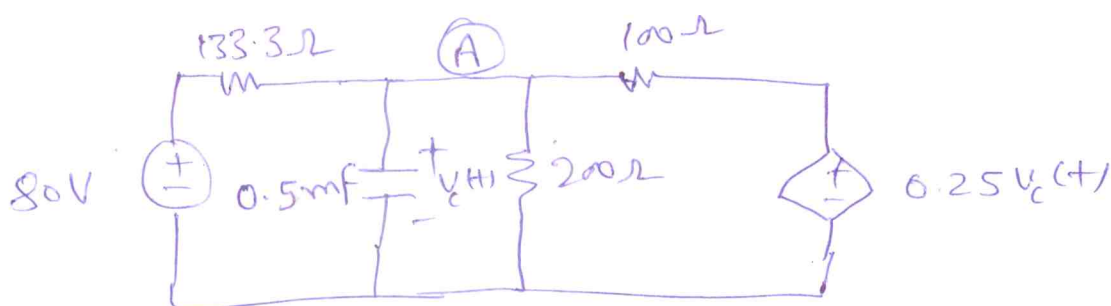

writing again KCL at node A

$$\frac{V_c(t) - 80}{133.3} + C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{200} + \frac{V_c(t) - 0.25 V_c(t)}{100} = 0$$

$$\frac{V_c(t) - 80}{133.3} + C \frac{dV_c(t)}{dt} + \frac{V_c(t)}{200} + \frac{0.75 V_c(t)}{100} = 0$$

$$\frac{V_c(t) - 80}{133.3} + C \frac{dV_c(t)}{dt} + \frac{V_c(t) + 1.5 V_c(t)}{200} = 0$$

$$\frac{V_c(t) - 80}{133.3} + C \frac{dV_c(t)}{dt} + \frac{2.5 V_c(t)}{200} = 0$$


$$0.025 \frac{dV_c(t)}{dt} + V_c(t) = 30$$

$$V_c(t) = 30 + 7.29 e^{-t'/0.025}$$

$$V_c(t) = 30 + 7.29 e^{-40t'}$$

where $t' = t - 0.06$

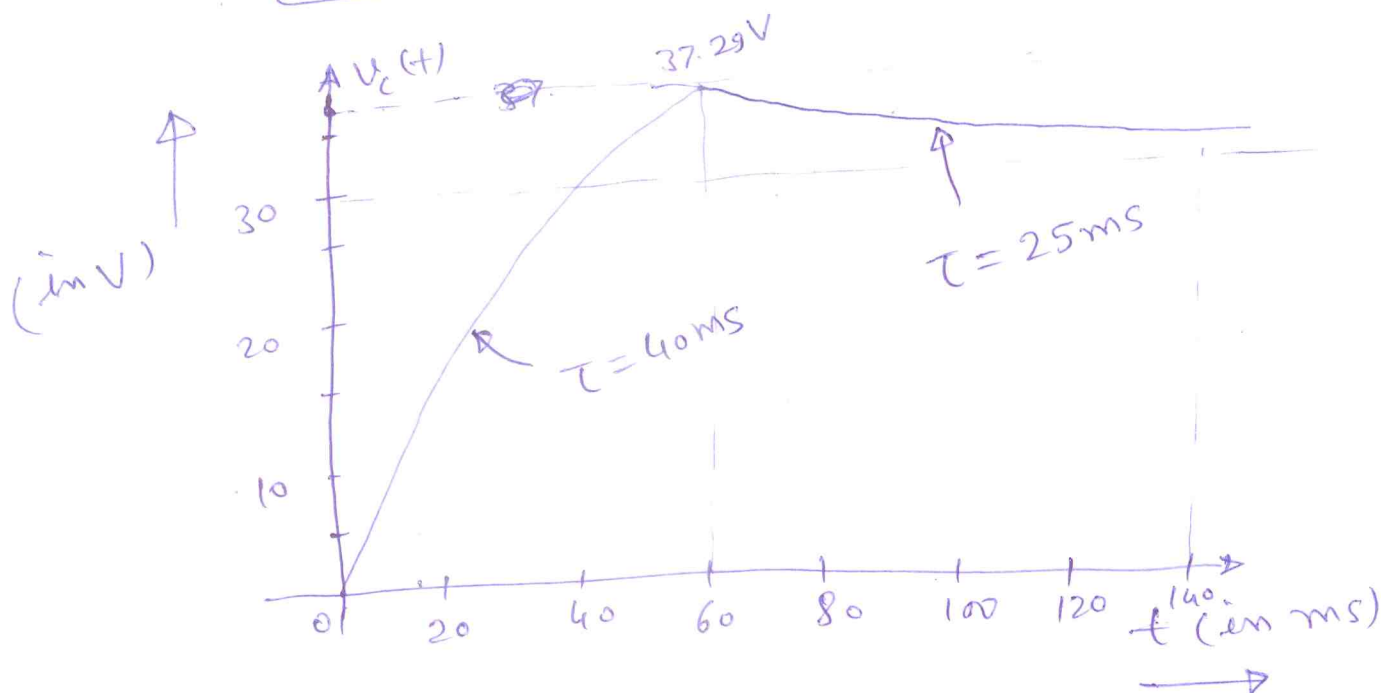
$$V_c(t) = 30 + 7.29 e^{-40(t-0.06)} \quad \text{for } t \geq 60 \text{ ms}$$




(9)

(6)

The $80 u(-t)$ waveform is as.

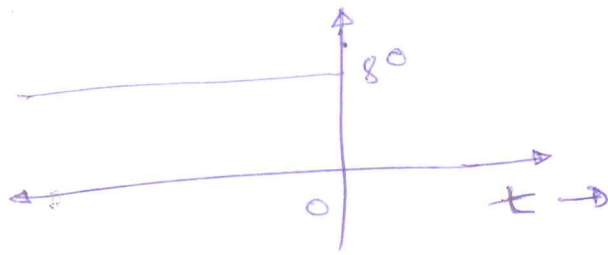

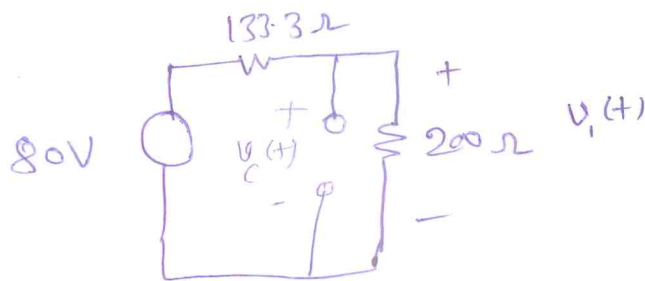At $t=0$ the capacitor will behave as open circuited due to connected to $80 V$ source a long time prior to $t=0$. Hence the circuit will be as follows at $t=0^-$.




Voltage across capacitor will be equal to voltage across 200Ω resistance. So.

$$V_1(t) = 80 \times \frac{200}{200 + 133.3} = 48 V.$$

$$\text{Hence } V_c(0^-) = V_c(0^+) = 48 V.$$

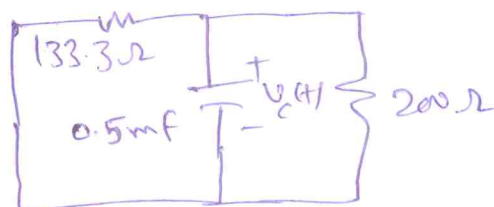
from ~~at~~ $t=0^+$ to $t=0.06 s$ the circuit will be as-



The resistance seen by the capacitor

$$R = \frac{200 \times 133.3}{200 + 133.3} = 80 \Omega$$

Hence the eq. circuit will be as.

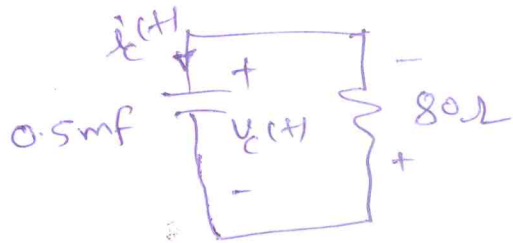

writing KVL in loop.

$$V_c(t) + 80 i_c(t) = 0.$$

$$V_c(t) + 80 C \frac{dV_c(t)}{dt} = 0$$

$$\int \frac{dV_c(t)}{V_c(t)} = \int \frac{-1}{80 \times 0.5 \times 10^{-3}} dt$$

$$\log V_c(t) = \frac{-1}{0.04} t + K$$

$$V_c(t) = \cancel{K e^{-25t}} \cdot K e^{-25t}$$

Again from Initial condition.


$$K = V_c(0^+) = 48V.$$

$$V_c(t) = 48 e^{-\frac{t}{0.04}} V, \quad 0 \leq t \leq 0.06 S$$

Now

$$V_c(t) = V_c(0.06) = 48 \cdot e^{-\left(\frac{0.06}{0.04}\right)} = \cancel{10.71} \cdot 10.71 V$$

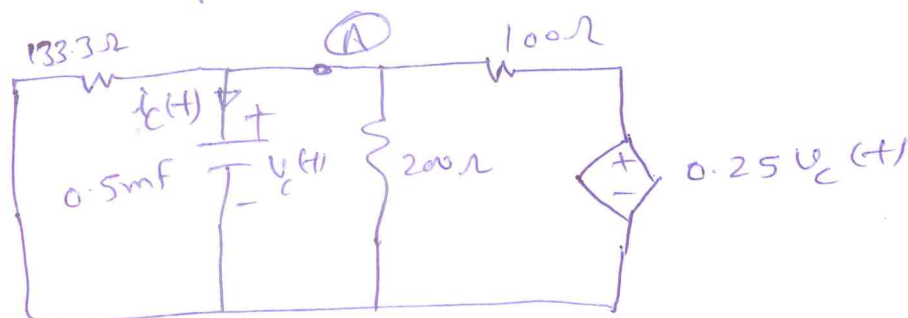Now $t = 60ms$ the switch is closed then the circuit topology will be.



writing KCL at node A.

$$\frac{V_c(t)}{133.3} + i_c(t) + \frac{V_c(t)}{200} + \frac{0.75 V_c(t)}{100} = 0.$$

$$0.02 V_c(t) + C \frac{dV_c(t)}{dt} = 0.$$

$$\int_{t=0.06}^t \frac{dV_c(t)}{V_c(t)} = \int_{t=0.06}^t -\frac{0.02}{C} dt$$

$$\left[\log V_c(t) \right]_{10.71}^{V_c(t)} = \frac{-0.02}{0.5 \times 10^{-3}} [t - 0.06]$$

$$\log [V_c(t)] - \log [10.71] = -40 [t - 0.06]$$

$$V_c(t) = 10.71 e^{-40(t-0.06)} \quad t \geq 0.06 \text{ s}$$

