

1) From, thevenin equivalent circuit, $R_T = 10k \parallel (10k + 5k) = 6k$


$$V_T = \frac{10 \times 15}{10 + 10 + 15} = 6V, \text{ thus } V_F = 6V; V_{in} = 0V$$

$$\text{Time constant, } \tau = R_T C = 6k \times 0.001 \times 10^{-6} = 6msec$$

$$V_c(t) = 6(1 - e^{-t/\tau}) V \text{ and } V_o(t) = V_c(t) \times \frac{5k}{5k + 10k} = 2(1 - e^{-\frac{t}{6 \times 10^{-6}}}) V$$

$f = 5kHz \Rightarrow T = \frac{1}{2f} = 100\mu sec$ where $T \gg 5\tau$, so steady state will be reached


for $t_1 < t < t_2$ (below)

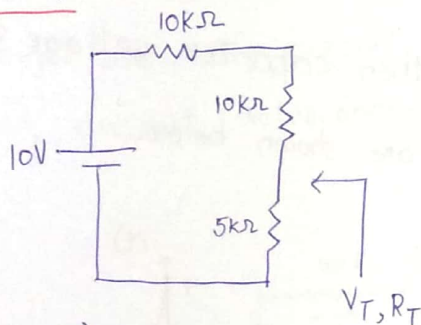

$$V_{in} = -V \times \frac{(R_2 + R_3)}{R_1 + R_2 + R_3} = -6V$$


$$V_F = V \times \frac{15}{25} = 6V \text{ and } V_o(t) = \frac{1}{3} \times \{ 6 + (-6 - 6)e^{-t/\tau} \} = 2 - 4e^{-t/\tau} V$$

for $t_2 < t < t_3$ (below)

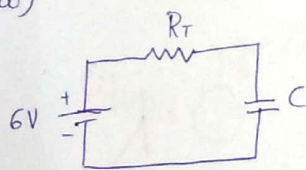

$$V_{in} = V \times \frac{15}{25} = 6V$$
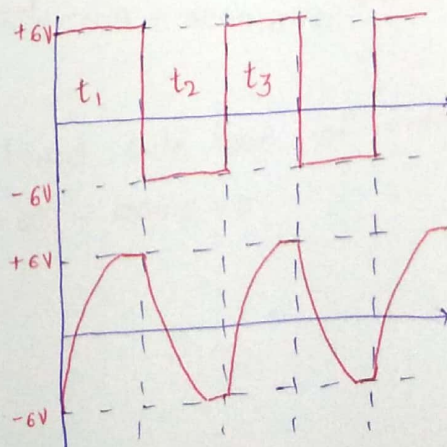
$$V_F = -V \times \frac{15}{25} = -6V \text{ and } V_o(t) = \frac{1}{3} \times \{ -6 + (12)e^{-t/\tau} \} = -2 + 4e^{-t/\tau} V$$



Q 2) $V_c = 0$ at $t=0$ and S_2 is open and S_1 is closed

$\tau = R_1 C = 10^{-3} \text{ sec}$ and $V_{in} = 0 \text{ V}$ and $V_F = 10 \text{ V}$ then

$$V_c(t) = 10(1 - e^{-t/\tau}) \quad \text{and} \quad i(t) = \frac{V}{R} e^{-t/\tau}$$





at $t = 2 \text{ msec}$, $V_c = 8.65 \text{ V}$ and $i = 0.135 \text{ mA}$

a) S_2 is closed at $t = 2 \text{ msec}$, then $R_T = 10 \text{ K} \parallel 10 \text{ K} = 5 \text{ K}$ and $V_T = 5 \text{ V}$
 So, $\tau = R_T C = 0.5 \text{ msec}$ and $V_{in} = 8.65 \text{ V}$, $V_F = 5 \text{ V} \Rightarrow V_c(t) = 5 + (8.65 - 5)e^{-\frac{(t-2)}{\tau}}$

$$\Rightarrow V_c(t) = 5 + 3.65 e^{-\frac{(t-2)}{\tau}} \text{ V}$$


$$\text{then, } i(t) = \frac{10 - V_c(t)}{10} = 0.5 - 0.365 e^{-\frac{(t-2)}{\tau}}$$

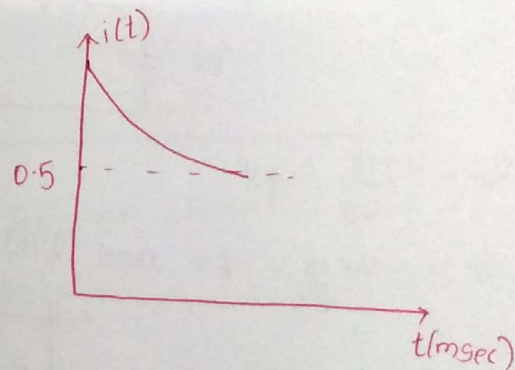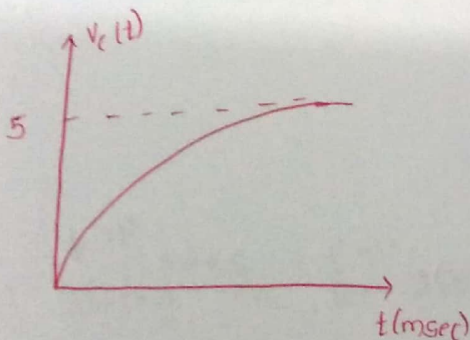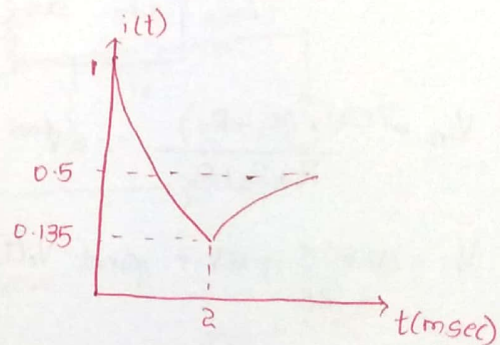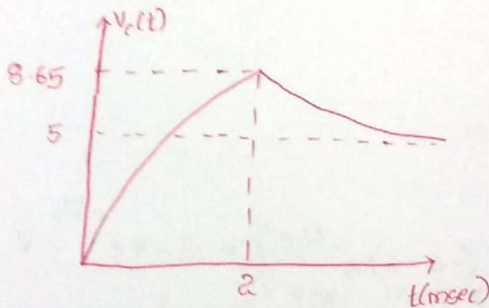b) S_2 is closed, when $V_c = 5 \text{ V}$, then capacitor voltage remains at 5 V
 therefore, $V_F = 5 \text{ V}$ and plots are shown below.



(3)

Q3) The interconnection is invalid

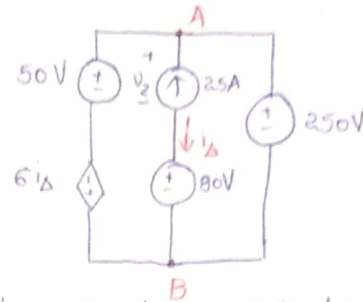

The current in the middle branch has to be $-25A$ because $25A$ current is flowing from B to A node


$$\text{So, } 6i_A = 6(-25) = -150V$$

$$V_{AB} = 50 - (-150) = 200V \text{ on left side of circuit}$$


$$V_{AB} = 250V \text{ on right side of circuit}$$

Therefore, circuit interconnection is valid.

4)

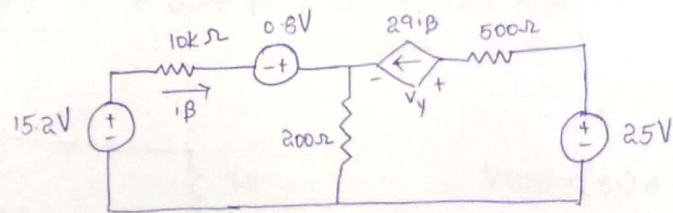

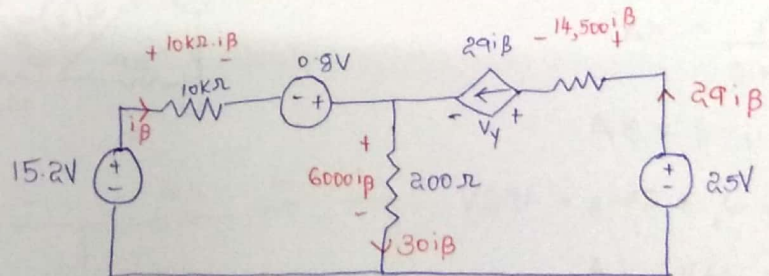current in the middle branch, $i_{200\Omega} = i_\beta + 29i_\beta = 30i_\beta$



a) Writing KVL for left-hand side loop of circuit

$$-15.2 + 10,000i_\beta - 0.8 + 6000i_\beta = 0$$

$$\Rightarrow i_\beta = 1mA$$

Writing KVL for right-hand side loop of circuit

$$-V_y - 14,500i_\beta + 25 - 6000i_\beta = 0$$

; wherein, $i_\beta = 1mA$

$$\Rightarrow \boxed{V_y = 4.5V}$$

b) We will be using power equation, $P = VI = \frac{V^2}{R} = I^2 R$

i) Power in 15.2V (voltage source) = $1 \times 15.2 = -15.2 \text{ mW}$

ii) Power in $10k\Omega$ (resistor) $= I^2 \times 10k\Omega = 10mW$

iii) Power in $0.8V$ (voltage source) $= -1 \times 0.8 = -0.8mW$

iv) Power in 200Ω (resistor) = $30^2 \times 200 = 180\text{mW}$

v) Power in dependent source = $29 \times 4.5 = 130.5 \text{ mW}$

vi) Power in 500Ω $= 29^2 \times 500 = 420.5 \text{ mW}$

vii) Power in $25V$

$$= -29 \times 25 = -725mW$$

∴ The total power generated in circuit is sum of negative power values $= -15.2 - 0.8 - 72.5 = \underline{-741 \text{ mW}}$

∴ The total power absorbed in circuit is sum of positive values

$$= 10 + 180 + 130.5 + 420.5 = 741 \text{ mW}$$
$$V_2 = 80 + 4(12) = 128 \text{ V}$$

$$V_1 = 120 - \{8 + 12 + 4\} \times 2 = 80V$$


$$i_1 = \frac{v_1}{6+10} = 5A$$

$$i_3 = i_1 - 2 = 3 \text{ A}$$

$$V_g = V_1 + 24i_3 = 152V$$

$$i_4 = 2 + 4 = 6 \text{ A}$$

$$I_g = -14 - 13 = -6 - 3 = -9A$$

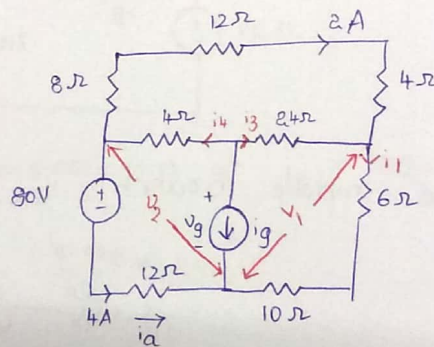

b) Power equation, $P = I^2 R$

$$P_{8\Omega} = (8) a^2 = 32W$$

$$P_{4\Omega} = (4)(2^2) = 16W$$

$$P_{24\Omega} = (24)(3)^2 = 216W$$

$$P_{\text{loss}} = (10)(5)^2 = 250 \text{ W}$$

$$P_{122} = (12)(2^2) = 48W$$

$$1 \quad P_{4\Omega} = (4)(6^2) = 144 \text{ W}$$

$$1 \quad P_{6\Omega} = (6)(5^2) = 150 \text{ W}$$

$$1 \quad P_{12\Omega} = (12)(4)^2 = 192W$$

(5)

c) $V_g = 152V$

d) Power absorbed by all resistors

$$\sum P_{\text{absorbed}} = 32 + 16 + 216 + 250 + 48 + 144 + 150 + 192 = 1048W$$

Power associated with voltage source

$$P_{\text{voltage-source}} = (80)(4) = 320W$$

$$\text{Power delivered by current source} = -V_g \cdot i_g = -(152)(9) = -1368W$$

Thus, total power dissipated is $1048 + 320 = 1368W$

and total power developed is $1368W$

6) $50i_2 + \frac{V_o}{50} + \frac{V_o}{12.5} = 0 \Rightarrow 50i_2 + \frac{250mV}{50\Omega} + \frac{250mV}{12.5} = 0$


$$\Rightarrow i_2 = -0.5mA$$

$$V_1 = i_2 \times 100 = -50mV$$

$$20i_1 + \frac{(-0.050)}{25} + (-0.0005) = 0 \Rightarrow i_1 = 125\mu A$$

$$V_g = 10i_1 + 40i_1 = 50i_1 \Rightarrow V_g = 6.25mV$$

7) For $t < 0$


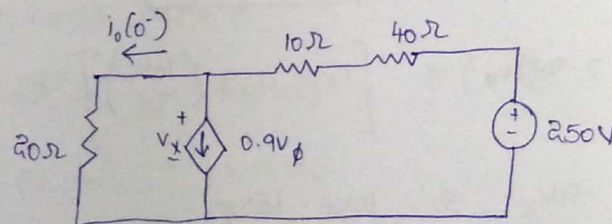


$$\frac{V_x}{20} + 9 \left[\frac{V_x - 250}{50} \right] + \left[\frac{V_x - 250}{50} \right] = 0$$


$$\Rightarrow V_x = 200V$$

$$i_o(0^-) = \frac{200}{20} = 10A$$


(6)

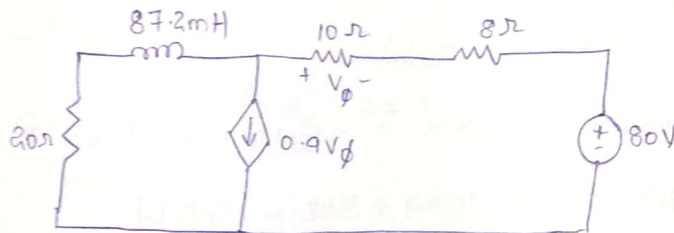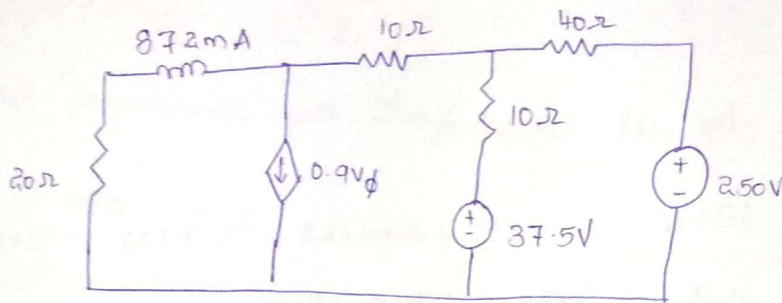 $t > 0$ 

Find thevenin equivalent w.r.t a, b

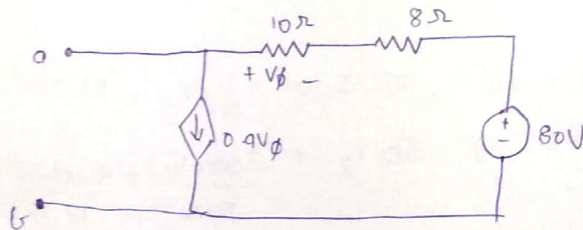
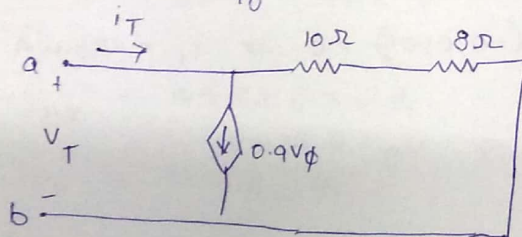
$$\frac{V_{Th} - 80}{18} + 9 \frac{(V_{Th} - 80)}{18} = 0 \Rightarrow V_{Th} = 80V$$



$$V_T = (i_T - 0.9V_T) 18 = \left[i_T - 0.9 \left(\frac{10V_T}{18} \right) \right] 18$$


$$V_T = 18i_T - 9V_T \Rightarrow 10V_T = 18i_T$$

$$\frac{V_T}{i_T} = R_{Th} = 1.8\Omega$$

$$i_o(\infty) = 80/21.8 = 3.67A$$


$$\tau = \frac{87.2}{21.8} \times 10^{-3} = 4ms; \quad 1/\tau = 250$$
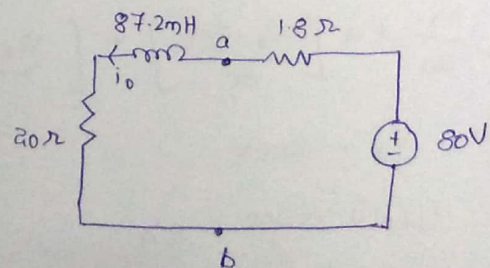
$$i_o = 3.67 + (10 - 3.67)e^{-250t} = 3.67 + 6.33e^{-250t}A, \quad t > 0$$




c) 8) For $t < 0$, $v_o(0) = 80V$

$t > 0$:

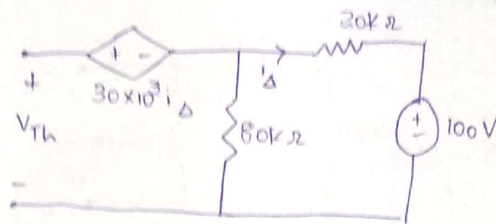

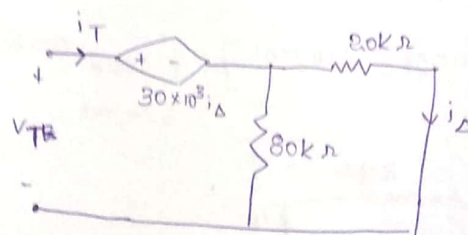
$$V_{Th} = 30 \times 10^3 i_D + 0.8(100) = 30 \times 10^3 \left(\frac{-100}{100 \times 10^3} \right) + 80 = 50V$$



$$V_T = 30 \times 10^3 i_D + 1.6 \times 10^3 i_T = 30 \times 10^3 (0.8) i_T + 1.6 \times 10^3 i_T = 40 \times 10^3 i_T$$

$$R_{Th} = \frac{V_T}{i_T} = 40k\Omega$$

$t > 0$

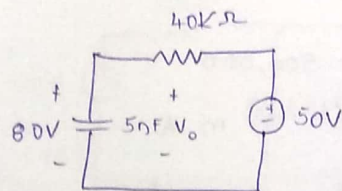

$$v_o = 50 + (80 - 50) e^{-t/\tau}$$

$$\tau = RC = (40 \times 10^3) (5 \times 10^{-9}) = 200 \times 10^{-6}; \quad 1/\tau = 5000$$

$$v_o = 50 + 30 e^{-5000t} V$$


11)

a)

$$0 \leq t \leq 2 \mu\text{sec}$$

$$i_L(0) = 0 ; i_L(\infty) = 5 \text{ mA}$$

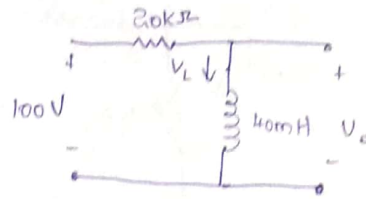
$$\tau = \frac{L}{R} = \frac{0.04}{20,000} = 2 \mu\text{s}$$



$$i_L = 5 - 5 e^{-500,000t} \text{ mA}, \quad 0 \leq t \leq 2 \mu\text{sec}$$

$$V_o = (0.04) \left[(500,000)(0.005) e^{-500,000t} \right] = 100 e^{-500,000t} \text{ V}, \quad 0 \leq t < 2 \mu\text{sec}$$

$$2 \mu\text{s} \leq t < \infty$$

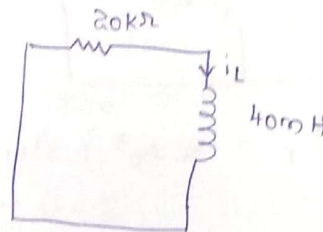

$$i_L(2 \mu\text{s}) = 5 - 5 e^{-1} \approx 3.16 \text{ mA}$$

$$i_L(\infty) = 0 ; \tau = 2 \mu\text{s} ; 1/\tau = 500,000$$

$$i_L = 0 + (3.16 - 0) e^{-500,000(t-2\mu\text{s})} \text{ mA}$$


$$= 3.16 e^{-500,000(t-2\mu\text{s})} \text{ mA}, \quad 2 \mu\text{s} \leq t < \infty$$

$$V_o = L \frac{di_L}{dt} = (0.04) (3.16 \times 10^{-3}) \left[-500,000 e^{-500,000(t-2\mu\text{s})} \right]$$

$$= (-5)(4)(3.16) e^{-500,000(t-2\mu\text{s})}$$

$$= -63.21 e^{-500,000(t-2\mu\text{s})} \text{ V}, \quad 2 \mu\text{s} \leq t < \infty$$

b)

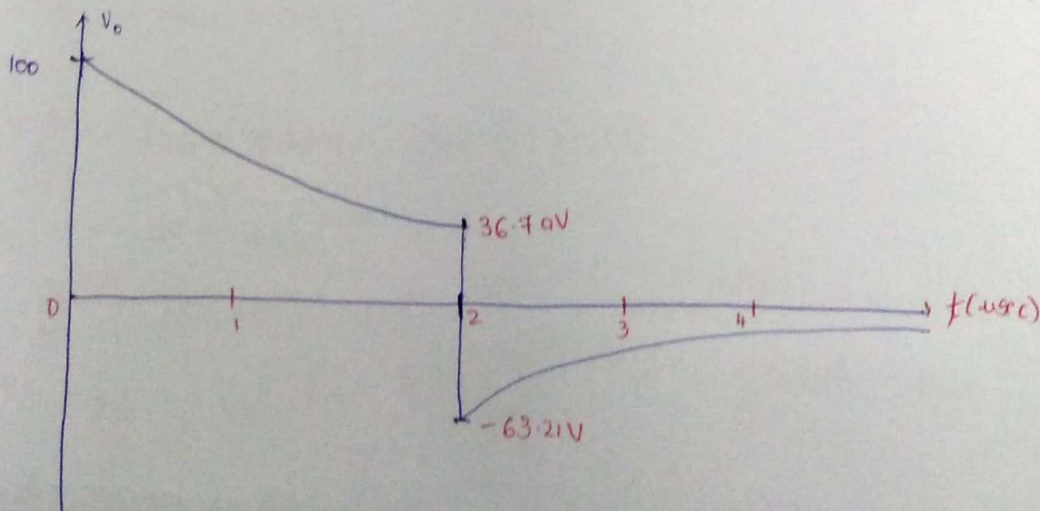

c) $v_o(4\text{ms}) = -23.25\text{V}$

$$i_o = \frac{23.25}{20,000} = 1.16\text{mA}$$

12)

a)

$$v_T = 2000 i_6$$


$$i_6 = \frac{6}{8} (i_T + \beta i_6)$$

$$i_6 = 0.75 i_T + 0.75 \beta i_6$$


$$\Rightarrow i_6 = \frac{0.75 i_T}{1 - 0.75 \beta} ; \quad 2000 i_6 = \frac{1500 i_T}{1 - 0.75 \beta}$$

$$R_{Th} = \frac{v_T}{i_T} = \frac{1500}{1 - 0.75 \beta} = -3000$$

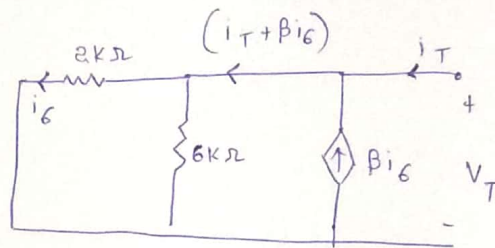
$$1 - 0.75 \beta = -0.5 \Rightarrow \beta = 2$$



b)

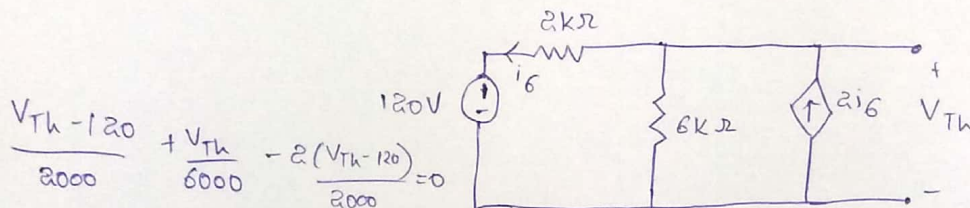

$$\Rightarrow v_{Th} = 180\text{V}$$

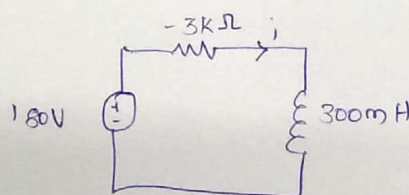

$$180 = -3000i + 0.3 \frac{di}{dt}$$

$$\Rightarrow \frac{di}{dt} = 600 + 10,000i = 10,000 (i + 0.06)$$

$$\Rightarrow i = -60 + 60 e^{10,000t} \text{ mA}$$

$$\frac{di}{dt} = (60 \times 10^3) (10,000) e^{10,000t} = 600 e^{10,000t}$$

$$v = 0.3 \frac{di}{dt} = 180 e^{10,000t} = 36,000 ; \quad e^{10,000t} = 200$$

$$t = \frac{\ln 200}{10,000} = 529.83 \mu\text{s}$$

$$13) V_{ph} = 400/\sqrt{3} = 231V$$

$$\text{load impedance per phase} = \frac{231}{30 \angle -30} = 7.7 \angle 30^\circ \Omega$$

$$\text{Total real power} = \sqrt{3} \times 400 \times 30 \times \cos 30^\circ = 18 \text{ kW}$$

$$\text{Total reactive power} = \sqrt{3} \times 400 \times 30 \times \sin 30^\circ = 10.392 \text{ KVAR}$$

$$W_A = W_{AB} =$$

$$W_A = V_{AB} I_A \cos(30^\circ + \theta) = 6 \text{ kW}$$

$$W_B = V_{AB} I_A$$

$$W_B = V_{AB} I_A \cos(30^\circ - \theta) = 12 \text{ kW}$$

$$14) V_{RY} = 400 \angle 0^\circ, V_{YB} = 400 \angle -120^\circ, V_{BR} = 400 \angle -240^\circ$$

$$I_{RY} = \frac{20000}{400} = 50 + 0j \text{ A}$$

$$I_{YB} = \frac{30,000}{400} \angle -120 - 36.86^\circ = 75 \angle -156.86^\circ \text{ A}$$

$$I_{BR} = \frac{20000}{400} \angle -240 - 53.13^\circ = 50 \angle -187^\circ \text{ A}$$

$$I_R = I_{RY} - I_{BR} = 99.82 \angle -3.4^\circ \text{ A}$$

$$I_Y = I_{YB} - I_{RY} = 122.56 \angle -166^\circ \text{ A}$$

$$I_B = I_{BR} - I_{YB} = 40.37 \angle 61.4^\circ \text{ A}$$

$$W_1 = V_{RY} I_R \cos \angle(V_{RY}, I_R) = 39.8 \text{ kW}$$

$$W_2 = V_{BY} I_B \cos \angle(V_{BY}, I_B) = 16.14 \text{ kW}$$

$$W_1 + W_2 = 56 \text{ kW}$$

$$15) 3V_{ph} I_{ph} \cos \theta = 5000 \text{ kW} ; I_{ph} = 360.8 \text{ A}$$

$$\text{Active component} = I \cos \theta = 288.7 \text{ A}$$

$$\text{Reactive component} = I \sin \theta = 216.5 \text{ A}$$

$$\text{At } 0.9 \text{ pf, New output} = \frac{500 \times 0.9}{0.8} = 5625 \text{ kW}$$