

Department of Electrical Engineering
Indian Institute of Technology Bombay, Powai
EE111 : Introduction to Electrical Engineering
Solution to Assignment 6

1. $E_p \approx V_p \approx 520V$
 $520 = 4.44 \times f \times N_p \times A_c \times B$ gives $B = 0.976 \text{Wb/m}^2$.
 $V_s = V_p \frac{N_s}{N_p} = 1300V$.

2. $8 \times N_p = 250$ gives $N_p = 32$
 $8 \times N_s = 3000$ gives $N_s = 375$
 $8 = 4.44 \times f \times B \times A_c$ gives $A_c = 0.01 \text{ sq. m.}$

3. $R'_2 = 0.009 \times \left(\frac{4400}{220}\right)^2 = 3.6\Omega$
 $X'_2 = 0.015 \times \left(\frac{4400}{220}\right)^2 = 6\Omega$
 $R_{1eq} = 7.05\Omega, X_{1eq} = 11.2\Omega$
Conversely, $R_{2eq} = 0.0176\Omega, X_{2eq} = 0.028\Omega$
Rated current in primary = $\frac{50 \times 10^3}{4400} = 11.36A$
Copper loss = $11.36^2 \times 7.05 = 910W$

4. $I_s = 80 \angle -36.87^\circ A$
Referred to secondary, $I'_s = 20 \angle -36.87^\circ A$
 $I_p = I_o + I'_s = 25 \angle -45^\circ - 20 \angle -36.87^\circ = 5.291 \angle -73.56^\circ$

5. $V_s = 500 \angle 0^\circ V, I_L = 200 \angle -36.87^\circ A$
 $V'_s = 500 \times 19.5 = 9750 \angle 0^\circ V$
 $R'_2 = 0.06 \times (19.5)^2 = 22.81\Omega$

$$X'_2 = 0.25 \times (19.5)^2 = 95.06\Omega$$

$$I'_L = 10.25\angle -36.87^\circ \text{ A}$$

$$V_o = V'_s + I'_L \times (R'_2 + jX'_2) = 10541\angle 3.47^\circ \text{ V}$$

$$I_o = 1.25\angle -60^\circ \text{ A}$$

$$I_p = I_o + I'_s = 11.41\angle -39.33^\circ \text{ A}$$

$$V_p = V_o + I_p \times (R_1 + jX_1) = 11543.71\angle 6.67^\circ \text{ V}$$

$$\text{Power factor angle} = 6.67 - (-39.33) = 46^\circ, P.f = 0.694$$

$$\text{Percentage efficiency} = \frac{500 \times 200 \times 0.8}{|V_p| \times |I_p| \times 0.694} \times 100 = 85.71\%$$

6. $R = 0.01 \text{ p.u.}, X = 0.05 \text{ p.u.}$

$$\text{Voltage regulation for } 0.8 \text{ p.f lag} = 0.01 \times 0.8 + 0.05 \times \sin(\cos^{-1}(0.8)) = 3.8\%$$

$$\text{Voltage regulation for } 0.8 \text{ p.f lead} = 0.01 \times 0.8 - 0.05 \times \sin(\cos^{-1}(0.8)) = -2.19\%$$

$$\text{Voltage regulation for UPF} = 0.01 \times 1.0 - 0.05 \times 0 = 1\%$$

8. $R_1 = 10\Omega, R_2 = 0.016\Omega, X_{1eq} = 34\Omega$

$$R'_2 = 10.88\Omega, R_{1eq} = 20.88\Omega$$

$$\text{Rated current in primary} = \frac{30 \times 10^3}{6000} = 5 \text{ A}$$

$$V_p^{sc} = 5 \times (R_{1eq} + jX_{1eq}) = 200\angle -58.44^\circ \text{ V}$$

$$\text{P.f} = 0.52 \text{ lag.}$$

9. Let full load Cu loss be x and iron loss be denoted by y

$$\text{At half load and } 0.8 \text{ p.f,}$$

$$0.25x + y = 500 \times 10^3 \times 0.8 \times (1 - 0.985)/0.985 = 6091.37 \text{ W}$$

$$\text{At full load and UPF,}$$

$$x + y = 1000 \times 10^3 \times (1 - 0.988)/0.988 = 12145.75 \text{ W}$$

$$\text{Solving, } x = 8072.50 \text{ W and } y = 4073.25 \text{ W}$$

$$\text{For maximum efficiency, Cu loss} = \text{Iron loss} = 4073.25 \text{ W.}$$

$$\text{This maximum efficiency will occur at } p \text{ times full load where}$$

$$p^2 \times 8072.50 = 4073.25, p = 0.71$$

$$\text{Maximum efficiency} = 98.86 \text{ \%}.$$

10. $V_{sc} = 60 \text{ V}, I_{sc} = 4 \text{ A}, P_{sc} = 100 \text{ W}$

$$P_{sc} = I_{sc}^2 R_{1eq}, \text{ gives } R_{1eq} = 6.25\Omega$$

$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = 15\Omega$$

$$X_{1eq} = \sqrt{Z_{sc}^2 - R_{1eq}^2} = 13.63\Omega$$

Full load current in the hv side = $\frac{10 \times 10^3}{2000} = 5$ A

$I_L = 5 \angle -36.87^\circ$ A, $V'_s = 2000 \angle 0^\circ$ V

$V_p = V'_s + I_L \times (R_{1eq} + jX_{1eq})$ gives $|V_p| = 2066$ V

11. Let full load Cu loss be x and iron loss be denoted by y

At half load and UPF,

$$0.25x + y = 300 \times 10^3 \times (1 - 0.92)/0.92 = 26086.96 \text{ W}$$

At full load and UPF,

$$x + y = 600 \times 10^3 \times (1 - 0.92)/0.92 = 52173.91 \text{ W}$$

Solving, $x = 34782.6$ W and $y = 17391.31$ W

At 60% load and UPF,

$$\text{Effeciency} = \frac{0.6 \times 600 \times 10^3}{0.6 \times 600 \times 10^3 + 17931.31 + 0.36 \times 34782.6} = 92.32\%$$