

Department of Electrical Engineering
 Indian Institute of Technology Bombay, Powai
 EE111 : Introduction to Electrical Engineering
 Solution to Assignment 4

1. $V_{ph} = 400/\sqrt{3} = 231 \text{ V}$

Load impedance per phase = $231/30\angle -30^\circ = 7.7\angle 30^\circ \Omega$

Total real power = $\sqrt{3} \times 400 \times 30 \times \cos 30^\circ = 18 \text{ kW}$

Total reactive power = $\sqrt{3} \times 400 \times 30 \times \sin 30^\circ = 10.392 \text{ kVAR}$

$W_A = V_{AB} I_A \cos(30^\circ + \theta) = 6 \text{ kW}$

$W_B = V_{AB} I_A \cos(30^\circ - \theta) = 12 \text{ kW}$

Delta Connected Load

$V_{AB} = 400\angle 0^\circ, V_{BC} = 400\angle -120^\circ, V_{CA} = 400\angle -240^\circ$

$I_{AB} = 400/7.7\angle 30^\circ = 52\angle -30^\circ \text{ A}, I_{BC} = 52\angle -150^\circ \text{ A}, I_{CA} = 52\angle -270^\circ \text{ A}$

$I_A = I_{AB} - I_{CA} = 90\angle -60^\circ \text{ A}, I_B = 90\angle -180^\circ \text{ A}, I_C = 90\angle -300^\circ \text{ A}$

$W_A = V_{AB} I_A \cos(30^\circ + \theta) = 18 \text{ kW}, W_C = 36 \text{ kW}$

2. $V_{phase} = V_{L-L} = 400 \text{ V}.$

Phase current = 20A. Therefore, Line current = $20\sqrt{3} \text{ A}.$

Total active power, $P = 3 \times 400 \times 20 \times \cos 40^\circ = 18385.06 \text{ W}$

Total reactive power, $Q = 3 \times 400 \times 20 \times \sin 40^\circ = 15426.9 \text{ VAR}$

Total VA = $\sqrt{P^2 + Q^2} = 24000$. Source capacity = 24000 VA.

Wattmeter 1, $W_1 = V_{AC} I_A \cos \angle V_{AC}, I_A$

Wattmeter 2, $W_2 = V_{BC} I_B \cos \angle V_{BC}, I_B$

$\angle V_{AC}, I_A = 70^\circ$

$$\angle V_{BC}, I_B = 10^\circ$$

Therefore, $W_1 = 4739.17 \text{ W}$ and $W_2 = 13645.89 \text{ W}$.

3. $V_{RY} = 400\angle 0^\circ$, $V_{YB} = 400\angle -120^\circ$, $V_{BR} = 400\angle -240^\circ$
 $I_{RY} = 20000/400 = 50 + j0 \text{ A}$, $I_{YB} = 30000\angle -120 - 36.86^\circ = 75\angle -156.86^\circ \text{ A}$,
 $I_{BR} = 20000\angle -240 - 53.13^\circ = 50\angle -187^\circ \text{ A}$
 $I_R = I_{RY} - I_{BR} = 99.82\angle -3.4^\circ \text{ A}$, $I_Y = I_{YB} - I_{RY} = 122.56\angle -166^\circ \text{ A}$, $I_B = I_{BR} - I_{YB} = 40.37\angle 61.4^\circ \text{ A}$
 $W_1 = V_{RY} I_R \cos \angle(V_{RY}, I_R) = 39857.7 \text{ W}$
 $W_2 = V_{BY} I_B \cos \angle(V_{BY}, I_B) = 16.14 \text{ kW}$
 $W_1 + W_2 = 56 \text{ kW}$

4. Converting delta to star

$$Z_{Yeq} = Z_{delta}/3 = 10 - j53.1\Omega$$

$$Z_{eq} = (20 + j37.7)/(10 - j53.1)\Omega = 68.39\angle 9.98^\circ\Omega$$

$$\text{Line current} = \text{phase current} = 398/(\sqrt{3} * 68.39) = 3.36 \text{ A}$$

$$\text{Power factor} = 0.985 \text{ lag}$$

$$\text{Real Power} = \sqrt{3} * V_L * I_L * \cos \theta = 2.28 \text{ kW}$$

$$\text{Reactive Power} = \sqrt{3} * V_L * I_L * \sin \theta = 397.83 \text{ VAR}$$

5. $3V_{ph}I_{ph} \cos \theta = 5000 \text{ kW}$

$$I_{ph} = 360.8 \text{ A}$$

$$\text{Active component} = I \cos \theta = 288.7 \text{ A}$$

$$\text{Reactive component} = I \sin \theta = 216.5 \text{ A}$$

$$\text{At } 0.9 \text{ power factor, new output} = 5000 * 0.9/0.8 = 5625 \text{ kW}$$

6. $\tan \theta = \sqrt{3}(W_B - W_C)/(W_B + W_C) = 1$, therefore $\theta = 45^\circ$

$$P = \sqrt{3} * V_L * I_L * \cos \theta$$

$$I_L = I_{ph} = (836 + 224)/(\sqrt{3} * 400 * \cos 45^\circ) = 2.16 \text{ A}$$

$$I_{AN} = V_{AN}/Z, \text{ therefore } Z = 106.95\angle 43^\circ\Omega$$

7. Phase voltage = $208/\sqrt{3} = 120$ V

$$I_A = V_{AN}/Z_A = 12 \text{ A}, I_B = 8\angle -150^\circ \text{ A}, I_C = 12\angle -210^\circ \text{ A}$$

$$I_N = -(I_A + I_B + I_C) = 5.67\angle 159^\circ \text{ A}$$

$$\text{Power input to phase A} = I_A^2 Z_A \cos \theta = 1440 \text{ W}$$

$$\text{Power input to phase B} = I_B^2 Z_B \cos \theta = 832 \text{ W}$$

$$\text{Power input to phase C} = I_C^2 Z_C \cos \theta = 1247 \text{ W}$$

$$\text{Total power} = 3579 \text{ W}$$

8. $Q = P \tan \phi$

$$\text{Total P} = 3450 \text{ kW}, \text{ Total Q} = 1137.5 \text{ kW}$$

$$\cos \phi = 0.95$$

$$S = \sqrt{P^2 + Q^2} = 3633 \text{ kVA}$$

$$\text{Load that the cable can carry at UPF} = 3633 \text{ kW}$$

9. Active power = $440 \times 40 \times 0.7 = 12320$ W

$$Q = 440 \times 40 \times \sin(\arccos 0.7) = 12569 \text{ VAR}$$

At 0.9 p.f lag, P remains the same.

$$Q \text{ supplied by capacitor} = 12569 - 12320 \tan(\arccos 0.7) = 6602 \text{ VAR}$$

$$X_C = V^2/6602, C = 108\mu\text{F}$$

10. Voltage across the lamp at u.p.f = $500/4 = 125$ V

$$\text{Voltage across the choke} = \sqrt{250^2 - 125^2} = 216.5 \text{ V}$$

$$2\pi fL = 216.5/4; L = 0.1723 \text{ H}$$

$$S = 250 \times 4 = 1000 \text{ VA}; Q = \sqrt{1000^2 - 500^2} = 866 \text{ VAR}$$

$$Q \text{ supplied by C} = 866 \text{ VAR}; C = 44\mu\text{F}$$